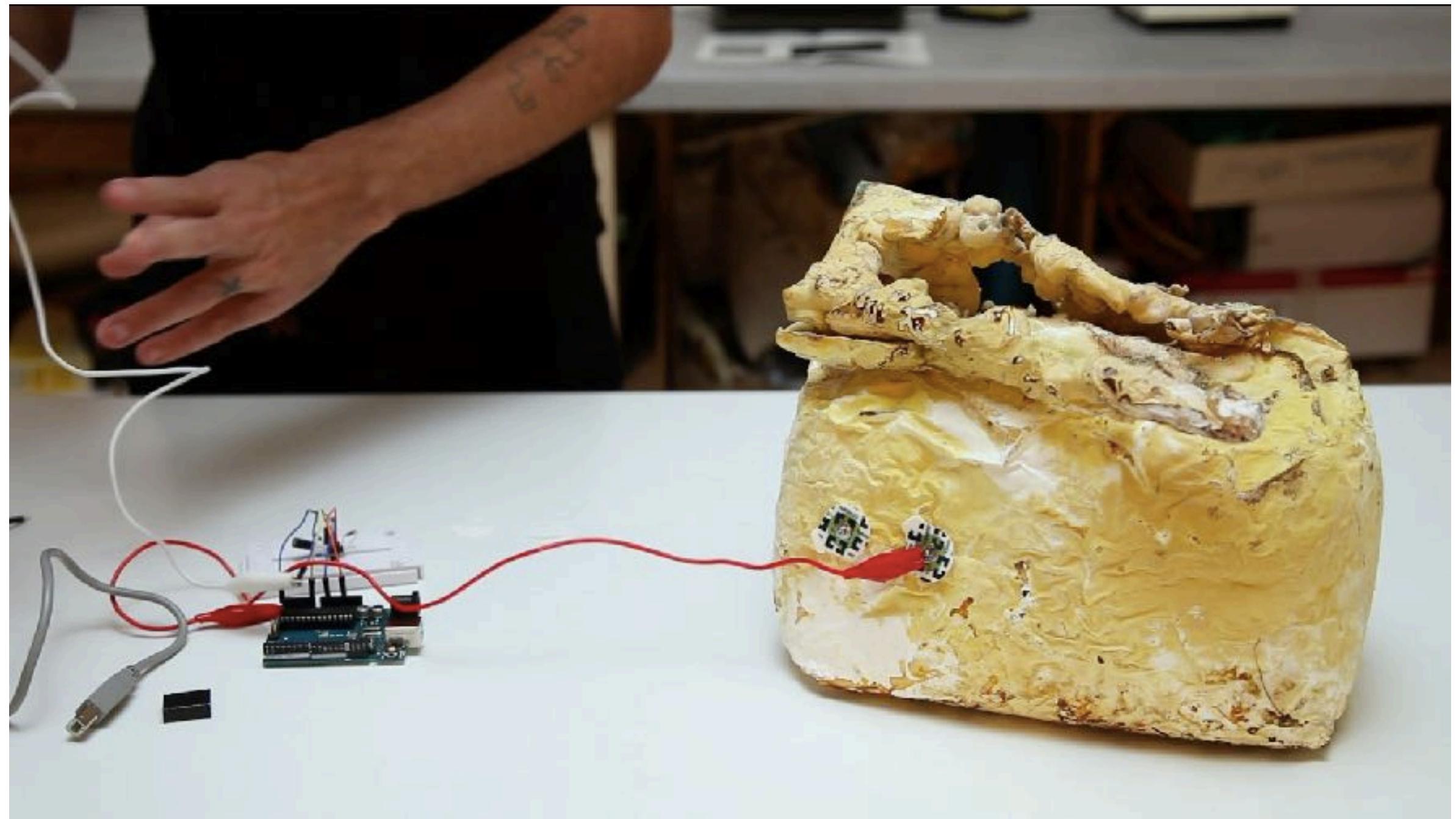


# Measurement of Electric Potentials in Plants

Mindaugas Gapševičius

# Motivation


This experiment offers insight into the electrochemical activity of living organisms such as plants, fungi, or even humans. By tracking a specimen over time—especially across the day—you may observe fluctuations in its bioelectric activity, reflecting internal and environmental changes. The experiment builds on Martin Howse's Interspecies Communication Platform



See for details: Kuni, V., Landwehr, D. Home  
Made Bio-Electronic Art
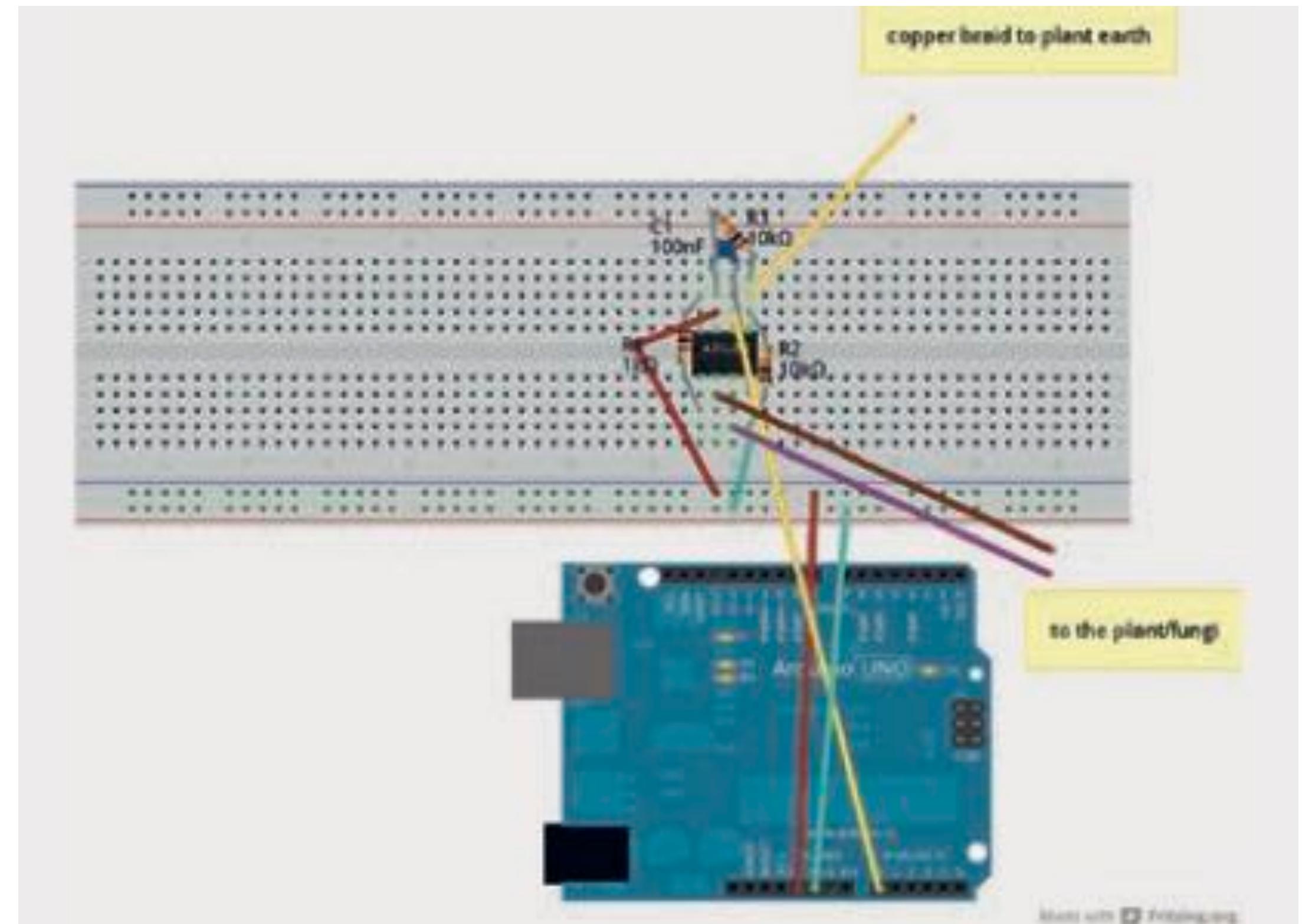
# Materials Needed

- Arduino microcontroller
- Breadboard
- $100 \mu\text{F}$  capacitor
- $1 \text{k}\Omega$  resistors ( $\times 3$ )
- Jumper wires
- USB cable
- Electrode patches
- AD620 instrumentation amplifier chip



# Experiment Setup

## 1. Preparing the Amplifier Circuit

- Place the AD620 amplifier chip on the breadboard so that its legs bridge the central gap.
- Insert the  $100\ \mu\text{F}$  capacitor between pin 4 (GND) and pin 7 (VCC) to stabilize the power supply from the Arduino.
- Place a  $1\ \text{k}\Omega$  resistor between pin 1 and pin 8 to set the gain (amplification factor) to approximately 50.
- Connect pin 7 to the 5V power of the Arduino and pin 4 to GND.

## 2. Establishing the Reference and Inputs

- Connect pin 5 (reference) to the organism being measured (e.g., plant or mycelium). This sets the amplifier's reference ground.
- Add the two remaining  $1\ \text{k}\Omega$  resistors to pin 5:
  - One connects to pin 7 (power),
  - The other to pin 4 (ground), forming a voltage divider that stabilizes the reference voltage.

# Experiment Setup

## 3. Signal Input & Output

- Connect pin 6 (output of the amplifier) to analog input Ao of the Arduino.
- Attach electrode patches to the organism and connect them to pins 2 and 3 of the AD620 chip (the differential input channels).


## 4. Arduino Connection and Software Setup

- Use the USB cable to connect the Arduino to your computer.
- Open the Arduino IDE, select your board and port under the "Tools" menu.
- Load the analog signal reading sketch:
- Navigate to File > Examples > Basics > AnalogReadSerial.
- Click the Upload button (right-pointing arrow) to upload the sketch to the board.
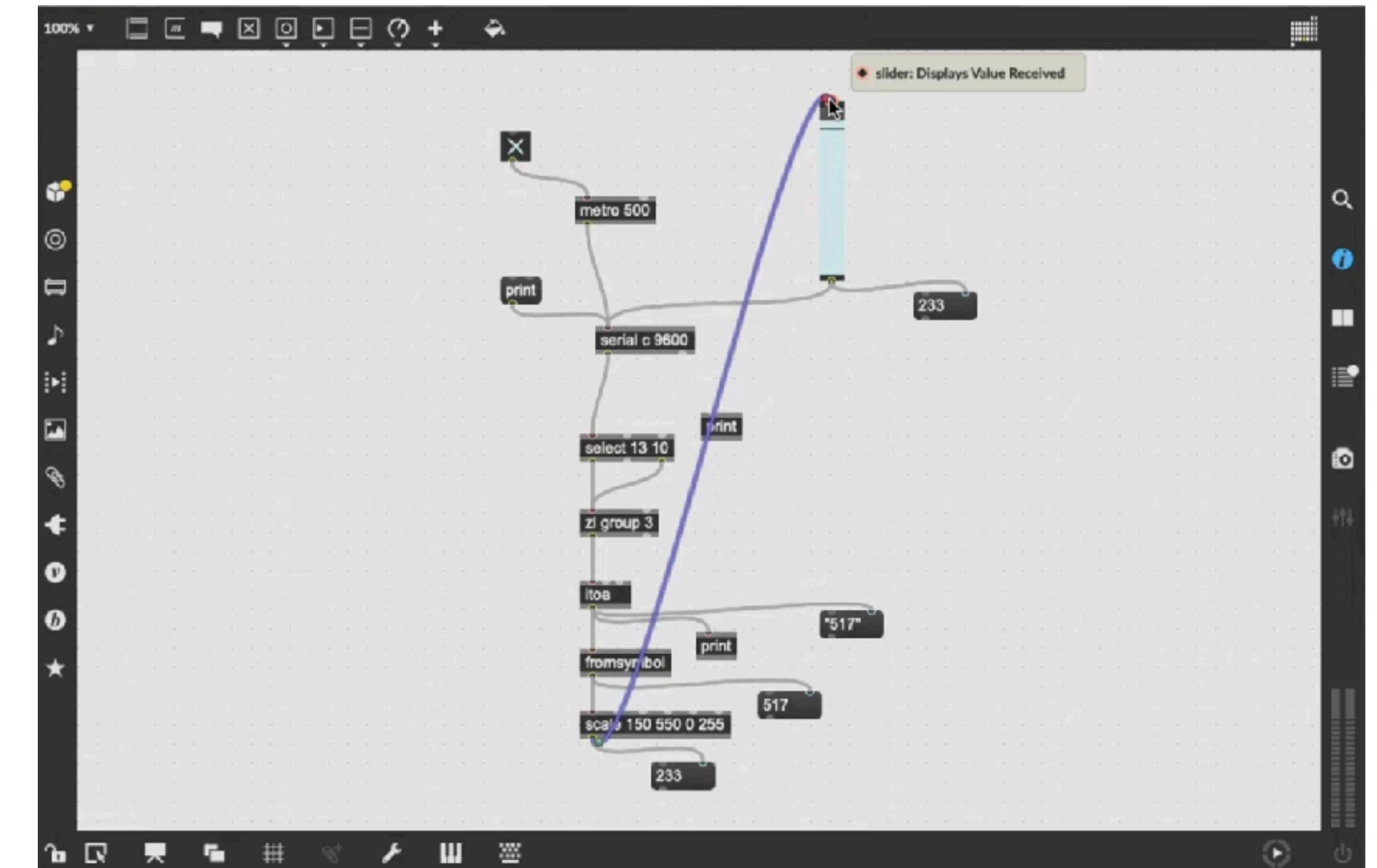
# Further steps

Once you've begun collecting electric potential data from your organism, you can start interpreting and visualizing it using visual programming environments. A quick and accessible entry point is to use platforms like Pure Data, Max/MSP, or TouchDesigner.

If you're new to Max/MSP, a concise tutorial on sensing and working with physical parameters is available here:  
[https://www.uni-weimar.de/kunst-und-gestaltung/  
wiki/GMU:Max\\_and\\_I,\\_Max\\_and\\_Me/  
Sensing\\_physical\\_parameters](https://www.uni-weimar.de/kunst-und-gestaltung/wiki/GMU:Max_and_I,_Max_and_Me/Sensing_physical_parameters)



# Summary

The short intro into the Measurement of Electric Potentials in Plants should have given you an idea of:

- How to track electrochemical signal from a living organism such as plant, human or bacteria
- How to convert this signal into digital signal (For that you use a microcontroller such as Arduino)
- How to convert the digital signal into sound (for that artists often use a visual programing framework such as Max/MSP, Pure Data, or TouchDesigner)

